數位系統技術




Lab 02 Full Adder 設計

Ren-Der Chen (陳仁德)
Department of Computer Science and
Information Engineering
National Changhua University of Education
E-mail: rdchen@cc.ncue.edu.tw
Spring, 2024


實驗目的

- 熟悉 Quartus 軟體之操作
- 學習如何以schematic方式設計half adder及full adder
- 學習如何對所設計之電路進行functional及timing simulation
- 學習如何將所設計之電路燒錄至FPGA晶片中,並利用實驗板週邊進行電路功能驗證


Get Started

 


Create a New Project

 


Create a New Project - add_half

 

Select a Device

 


Design Example: Half Adder

 


cout


Use Block Editor for Schematic Design

 


Import Logic Gates

 


Select and Import an AND2 Gate

 


An AND2 Gate is Imported

 


Select and Import an XOR Gate

 


An XOR Gate is Imported

 


Select and Import an Input Pin

 


Two Input Pins are Imported

 


Select and Import an Output Pin

 


Two Output Pins are Imported

 


Assign Names to I/O Pins

 

Connect Nodes with Wires

 


Save the Schematic File

 

Synthesize the Schematic Circuit


- The synthesis tool translates the schematic into logic expressions.
- Then the technology mapping step determines how each logic expression should be implemented in the logic elements (LEs) available in the target chip.
- The *Analysis* & *Synthesis* function performs the synthesis step.
- It produces a circuit of logic elements, where each element can be directly implemented in the target chip.

 
Run "Analysis & Synthesis" for Functional Simulation




```
Type ID Message
Running Quartus Prime Analysis & Synthesis
Command: quartus_map --read_settings_files=on --write_settings_files=off add_half -c add_half
18236 Number of processors has not been specified which may cause overloading on shared machines. 9
20030 Parallel compilation is enabled and will use 8 of the 8 processors detected
12021 Found 1 design units, including 1 entities, in source file add_half.bdf
12127 Elaborating entity "add_half" for the top level hierarchy
286030 Timing-Driven Synthesis is running
16010 Generating hard_block partition "hard_block:auto_generated_inst"
21057 Implemented 6 device resources after synthesis - the final resource count might be different
Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning
```

Create a Waveform File

 


 


Set End Time for Simulation

 


Insert Node for I/O Signals (1/3)

 


 


Insert Node for I/O Signals (2/3)

 


Insert Node for I/O Signals (3/3)

 


Set Values for Input Signals (1/2)

 


Set Values for Input Signals (2/2)

 

Save the Waveform File

 

 

Simulation


Functional simulation


- Logic elements and interconnection wires are perfect, causing no delay in propagation of signals through the circuit.
- Used to verify the functional correctness of a circuit.
- Takes much less time.

Timing simulation


Takes all propagation delays into account.

Set Simulation Tool - ModelSim

 

 

 
Check Functional Simulation Netlist (1/2)




Check Functional Simulation Netlist (2/2)

Name:	Setting:
Architecture name in VHDL output netlist	structure
Bring out device-wide set/reset signals as ports	Off
Disable detection of setup and hold time violations in the input registers of bi-directional pins	Off
Do not write top level VHDL entity	Off
Flatten buses into individual nodes	Off
Generate functional simulation netlist	On
Generate third-party EDA tool command script for RTL functional simulation	Off
Generate third-party EDA tool command script for gate-level simulation	Off
Maintain hierarchy	Off
Truncate long hierarchy paths	Off


Modify ModelSim Script

 


Run Functional Simulation

 


Functional Simulation Result

 

 
Perform Advanced Compilation for Timing Simulation




Modify ModelSim Script

 


Run Timing Simulation

 

Timing Simulation Result

 


Create the HDL (Verilog) File

 


Content in add_half.v (Generated by Tool)

```
module add half(
    a,
    b,
    cout,
    sum
input wire a;
input wire b;
output wire cout;
output wire sum;
assign cout = a & b;
assign sum = a ^ b;
endmodule
```

Create the Symbol File

 

Close the Current Project

 


All add_half files

data (D:) > csie_lab > lab02 > add_half

名稱	修改日期	類型
db	2022/2/28 下午 11:48	檔案資料夾
incremental_db	2022/2/28 下午 10:36	檔案資料夾
output_files	2022/2/28 下午 11:42	檔案資料夾
simulation	2022/2/28 下午 11:19	檔案資料夾
🔁 add_half	2022/2/28 下午 10:09	BDF 檔案
add_half	2022/2/28 下午 11:52	BSF 檔案
🛐 add_half	2022/2/28 下午 09:29	QPF 檔案
add_half.qsf	2022/2/28 下午 11:48	QSF 檔案
add_half.v	2022/2/28 下午 11:48	V 檔案
add_half.vwf	2022/2/28 下午 11:41	VWF 檔案

Design Example: Full Adder (1/2)

 


ab\cin	0	1
00	0	1
01	1	0
11	0	1
10	1	0


0

ab\cin


Design Example: Full Adder (2/2)

 


Create a New Project - add_full

 


Create a Schematic Design for add_full

 


Select and Import a Half Adder

 


Two Half Adders are Imported

 


Import OR2 Gate and I/O Pins

 

Add the add half Schematic File

 

Functional Simulation Result

 

Content in add_full.v (Generated by Tool)

```
add half
                                   b2v inst(
                            .a(a),
                            .b(b),
                            .cout (SYNTHESIZED WIRE 2),
module add full(
                            .sum(SYNTHESIZED WIRE 0));
    a,
    b,
    cin,
                       add half
                                   b2v inst1(
    cout,
                           .a(SYNTHESIZED WIRE 0),
    sum
                            .b(cin),
);
                            .cout (SYNTHESIZED WIRE 1),
                            .sum(sum));
input wire a;
                       assign cout = SYNTHESIZED WIRE 1 | SYNTHESIZED WIRE 2;
input wire b;
input wire cin;
output wire cout;
                       endmodule
output wire sum;
        SYNTHESIZED WIRE 0;
wire
        SYNTHESIZED WIRE 1;
wire
wire
        SYNTHESIZED WIRE 2;
```

Pin Assignments

Inputs






Outputs

LED1 LED0




$$\{cout, sum\} = a + b + cin$$

Start Compilation

 


Make Pin Assignments

 


Node Name	Direction	Location	I/O Bank	VREF Group	itter Locatior
in a	Input	PIN_D12	7	B7_N0	PIN_Y5
in_ b	Input	PIN_C11	7	B7_N0	PIN_AA2
in_ cin	Input	PIN_C10	7	B7_N0	PIN_AA1
out cout	Output	PIN_A9	7	B7_N0	PIN_W3
out sum	Output	PIN_A8	7	B7_N0	PIN_U6

Start Compilation

 

Program into Device

 

Verify Your Design

- sw2/sw1/sw0 : dn/dn/dn (0/0/0) => L1/L0: off/off (0/0)
- sw2/sw1/sw0 : dn/dn/up (0/0/1) => L1/L0: off/on (0/1)
- sw2/sw1/sw0 : dn/up/dn (0/1/0) => L1/L0: off/on (0/1)
- sw2/sw1/sw0 : dn/up/up (0/1/1) => L1/L0: on/off (1/0)
- sw2/sw1/sw0 : up/dn/dn (1/0/0) => L1/L0: off/on (0/1)
- sw2/sw1/sw0 : up/dn/up (1/0/1) => L1/L0: on/off (1/0)
- sw2/sw1/sw0 : up/up/dn (1/1/0) => L1/L0: on/off (1/0)
- sw2/sw1/sw0 : up/up/up (1/1/1) => L1/L0: on/on (1/1)

SW2 SW1 SW0



實驗報告

■ 請老師or助教驗證add_full電路之模擬波形及實驗板之行 為是否正確